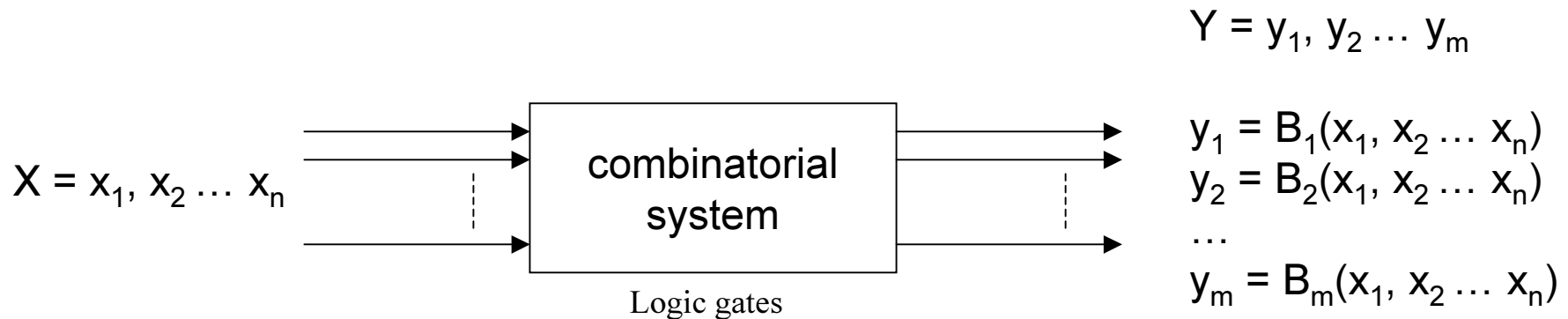


# Combinatorial systems



$$Y = B(X)$$

$B_x$  – boolean functions

Any change of input signal  $X$  modifies the output signal  $Y$  with maximum speed limited by the signal propagation time.

Output vector  $Y$  is a function of current value of  $X$  in any moment.

# Combinatorial systems - description

np.

$$y(a, b, c) = a*(b+\bar{c}) + (\bar{a}+b)*c$$

Truth table

a	b	c	y(a, b, c)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Sum of maxterms

$$y(a, b, c) = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c} + abc$$

Product of minterms

$$y(a, b, c) = (a+b+c) (a+\bar{b}+c) (\bar{a}+b+\bar{c})$$

Optimization algorithms of boolean functions !

# ***Boolean algebra***

Identity element

$$a+0=a$$

$$a*1=a$$

Commutativity

$$a+b=b+a$$

$$a*b=b*a$$

Associativity

$$a+(b+c)=(a+b)+c$$

$$a*(b*c)=(a*b)*c$$

Distributivity

$$a+(b*c)=(a+b)*(a+c)$$

$$a*(b+c)=(a*b)+(a*c)$$

Complement

$$a+\bar{a}=1$$

$$a*\bar{a}=0$$

Idempotency

$$a+a=a$$

$$a*a=a$$

Complement

$$a+1=1$$

$$a*0=0$$

Absorption

$$a+a*b=a$$

$$a*(a+b)=a$$

Element Elimination

$$a+\bar{a}*b=a+b$$

$$a*(\bar{a}+b)=a*b$$

De Morgan's Laws

$$\overline{a+b}=\bar{a}*\bar{b}$$


$$\overline{a*b}=\bar{a}+\bar{b}$$

# Logic gates



NOT

$$F = \bar{a}$$

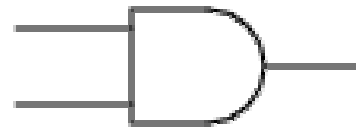


AND

$$F = a \cdot b$$



OR

$$F = a + b$$

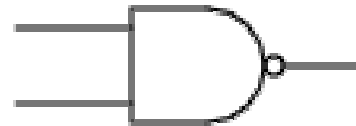

NAND

$$F = \overline{a \cdot b}$$



NOR

$$F = \overline{a + b}$$



XOR








$$F = a \oplus b$$




XNOR

$$F = \overline{a \oplus b}$$

# Realisation of boolean functions

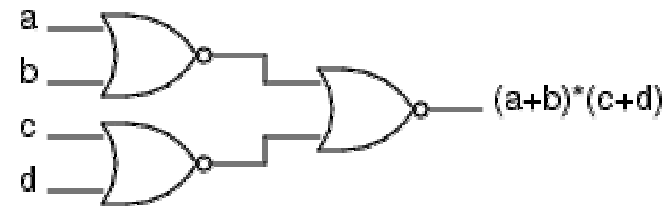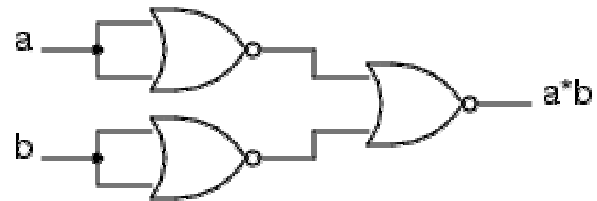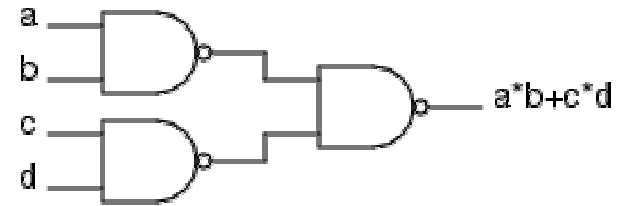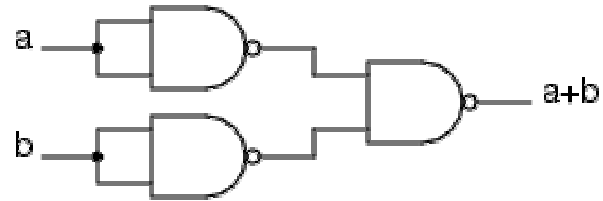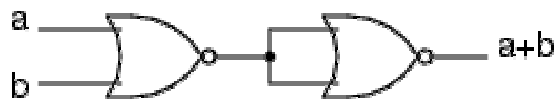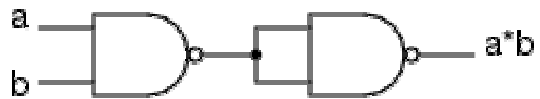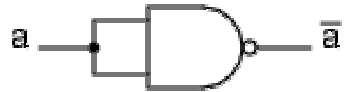


# Multiplexers

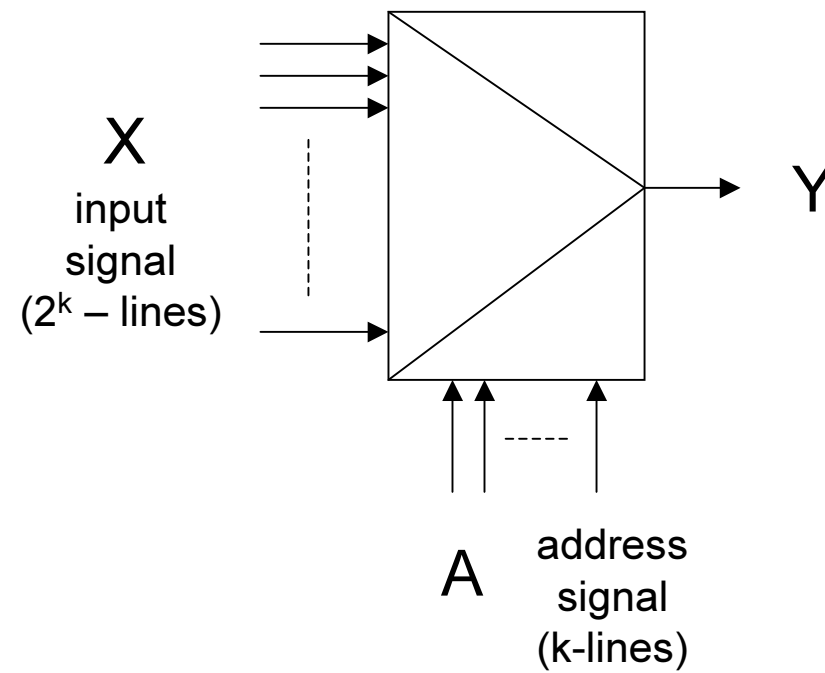


$$Y = x_0 \cdot \overline{a_{k-1}} \cdot \dots \cdot \overline{a_1} \cdot \overline{a_0} + x_1 \cdot \overline{a_{k-1}} \cdot \dots \cdot \overline{a_1} \cdot a_0 + \dots + x_{2^k-1} \cdot a_{k-1} \cdot \dots \cdot a_1 \cdot a_0$$


# ***Multiplexer 2x1***

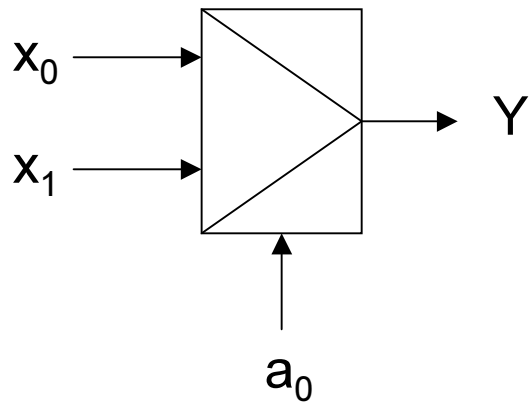
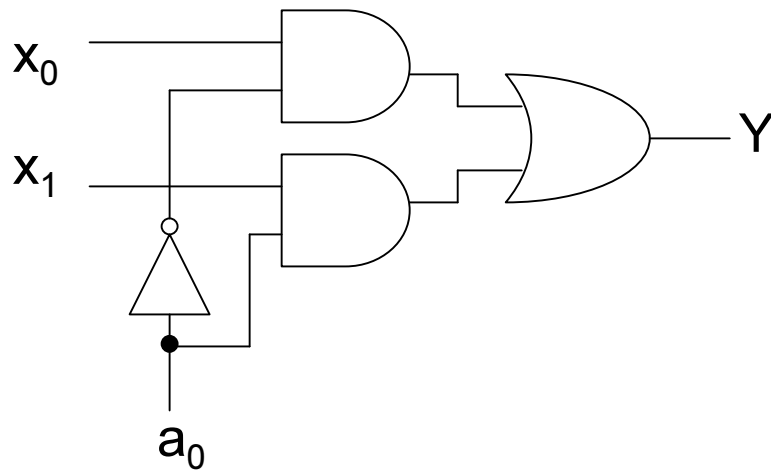
$$Y = x_0 \cdot \overline{a_0} + x_1 \cdot a_0$$



# Demultiplexers

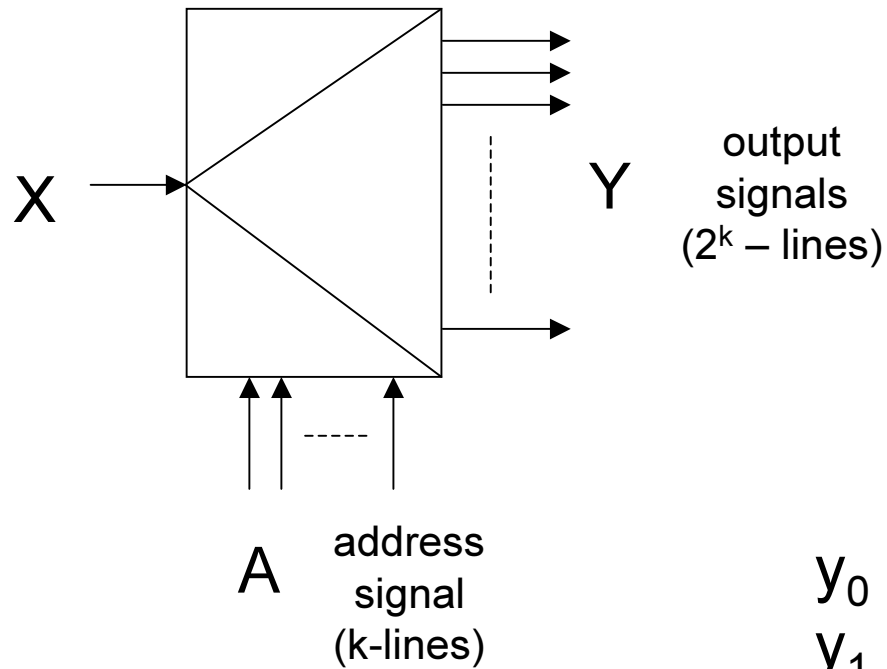


$$y_0 = X \cdot \overline{a_{k-1}} \cdot \dots \cdot \overline{a_1} \cdot \overline{a_0}$$
$$y_1 = X \cdot \overline{a_{k-1}} \cdot \dots \cdot \overline{a_1} \cdot a_0$$

...


$$y_{2^k-1} = X \cdot a_{k-1} \cdot \dots \cdot a_1 \cdot a_0$$




# ***Demultiplexer 1x2***

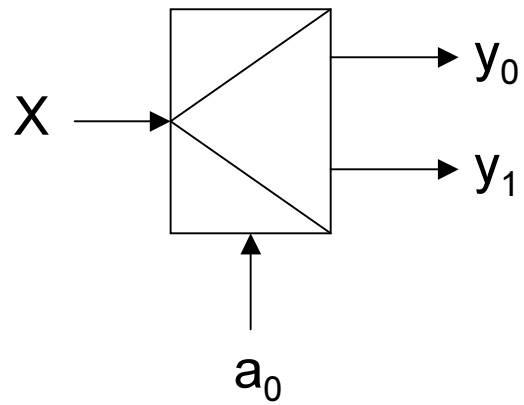

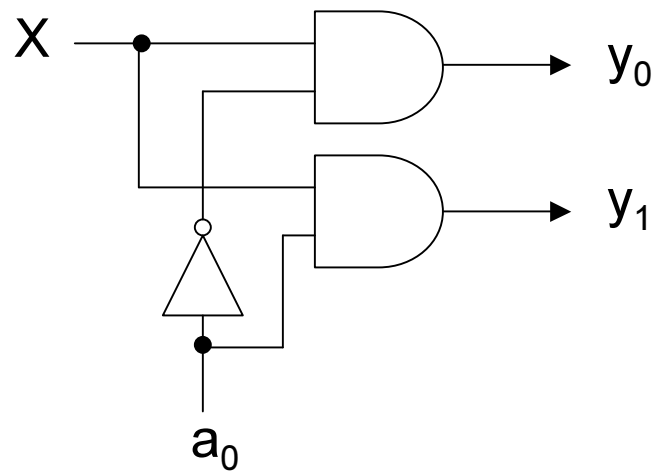
$$y_0 = X \cdot \overline{a_0}$$
$$y_1 = X \cdot a_0$$



# ***Cascades of (de)multiplexers***

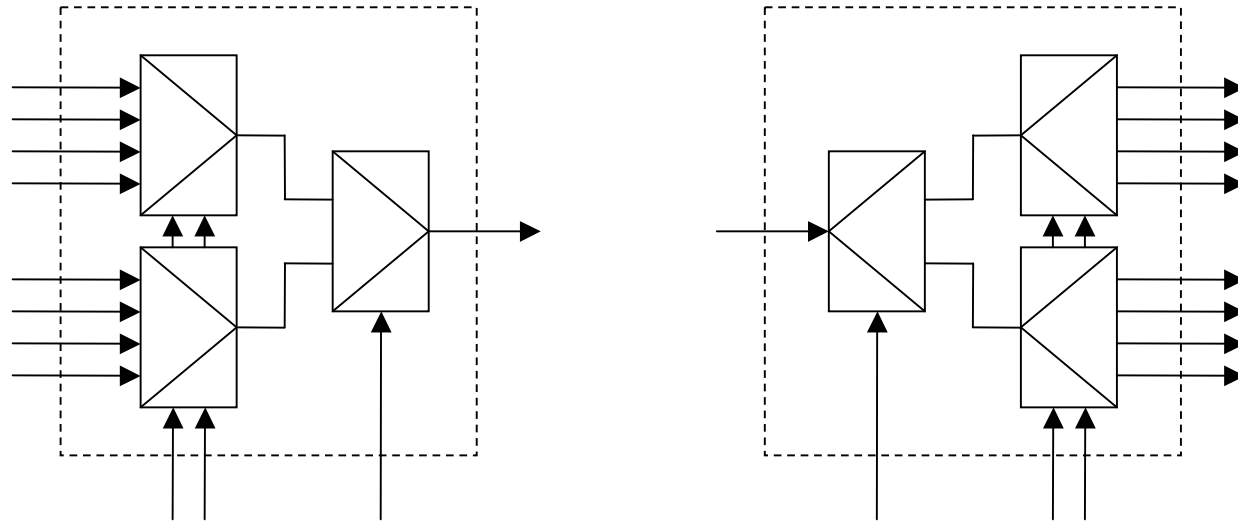

# State machines

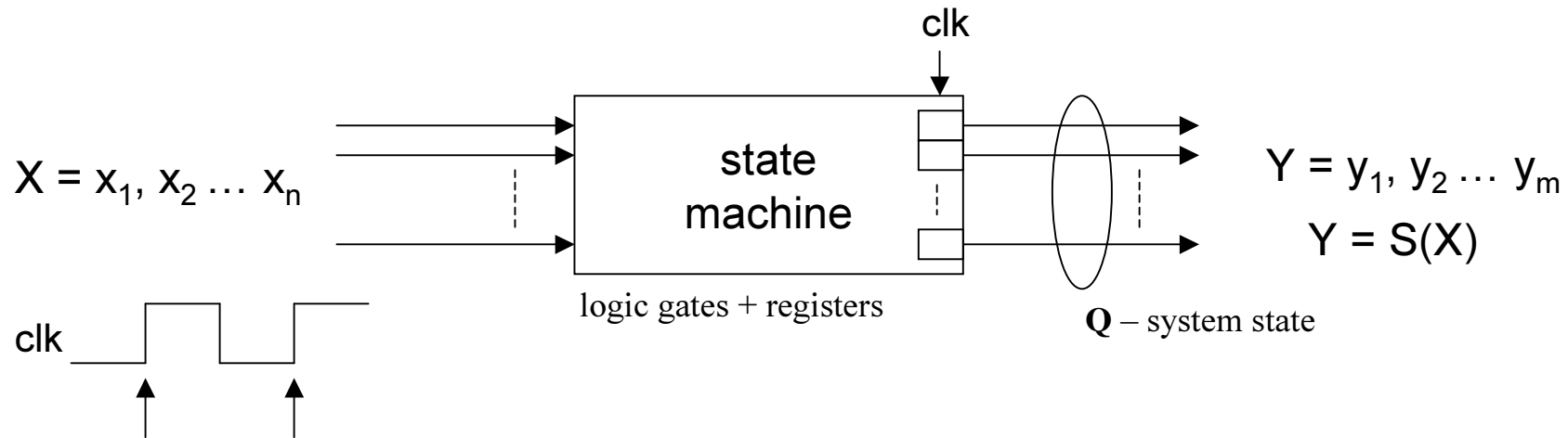


Any change of output signal  $Y$  is only possible at the change of the clock signal to memory elements (edge triggered write operation)

Output signals  $Y$  (when changed) are the function of input signal  $X$  only in the moment of the clock edge. In any other moment, the output  $Y$  is stable and independent of any change in input  $X$ .

Description of state machine consists in enumerating the output states  $Q$  and the sequence of their change (state diagram).

# ***State machine with feedback***

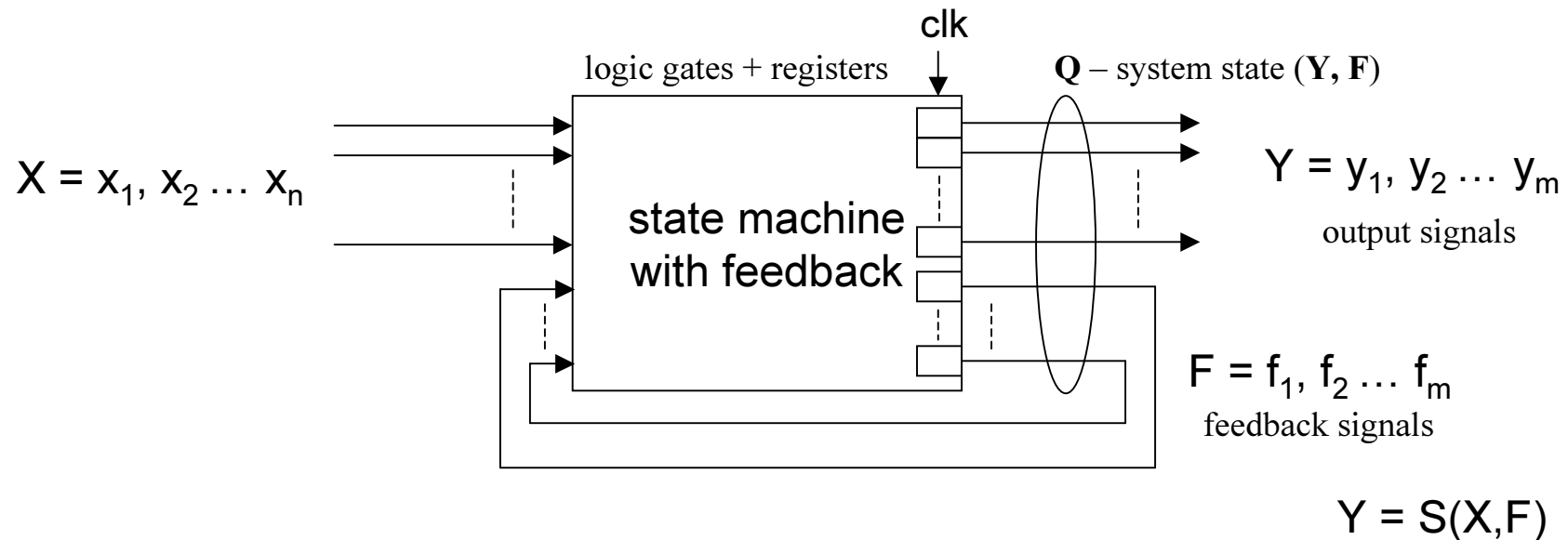


Change of  $Y$  (and  $Q$ ) is synchronised with clock signal.

Next state of the system depends on current input signals  $X$  and on current system state  $F$  (feedback).

System state can be described by set of values  $Y, F$  and sequence of their change (state diagram).



# State diagrams

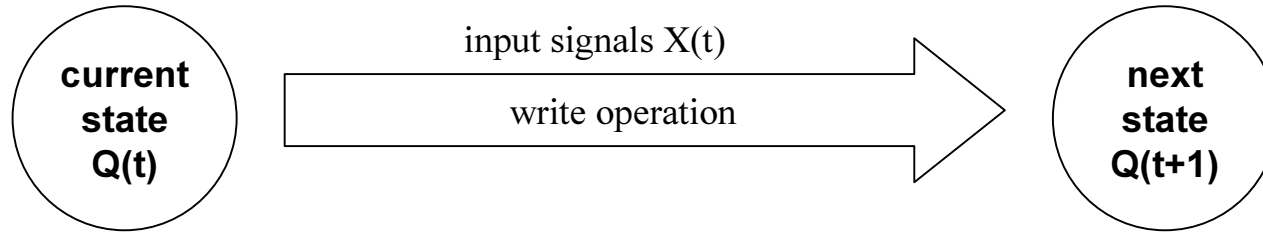

Next state depends on:


- 1) current state (signals Y, F)
- 2) input signals at the moment of write

## Example

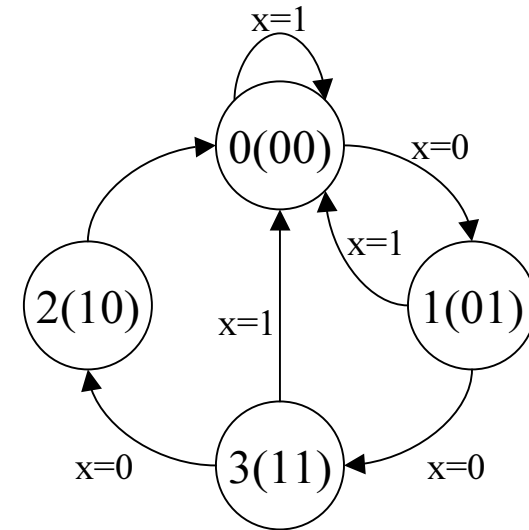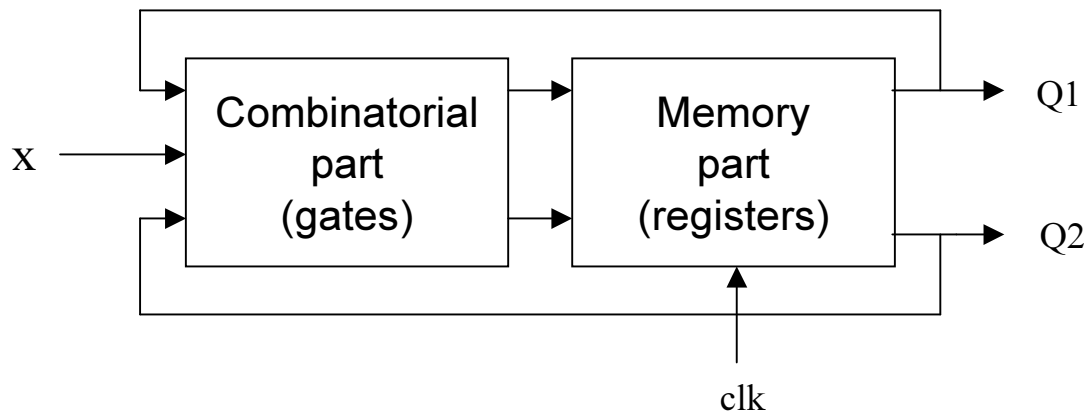


# State diagrams - examples

JK Flip-flop


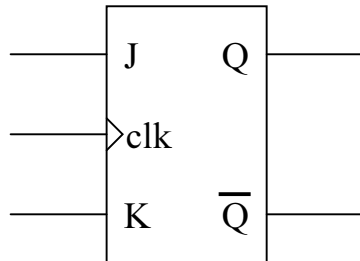


J(t)	K(t)	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

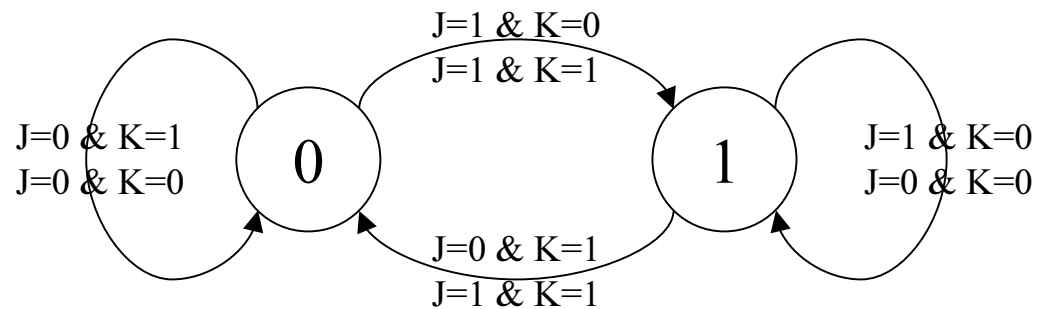
$$Q(t+1) = J(t) \bar{Q}(t) + \bar{K}(t) Q(t)$$





# State diagrams - examples

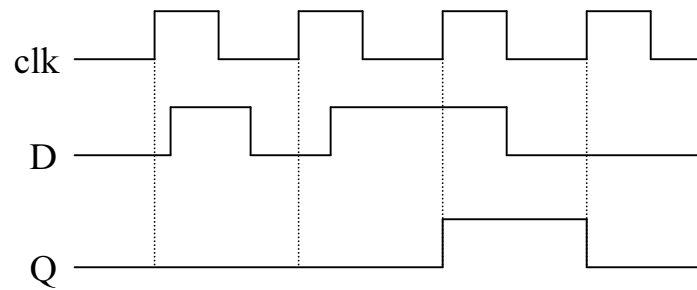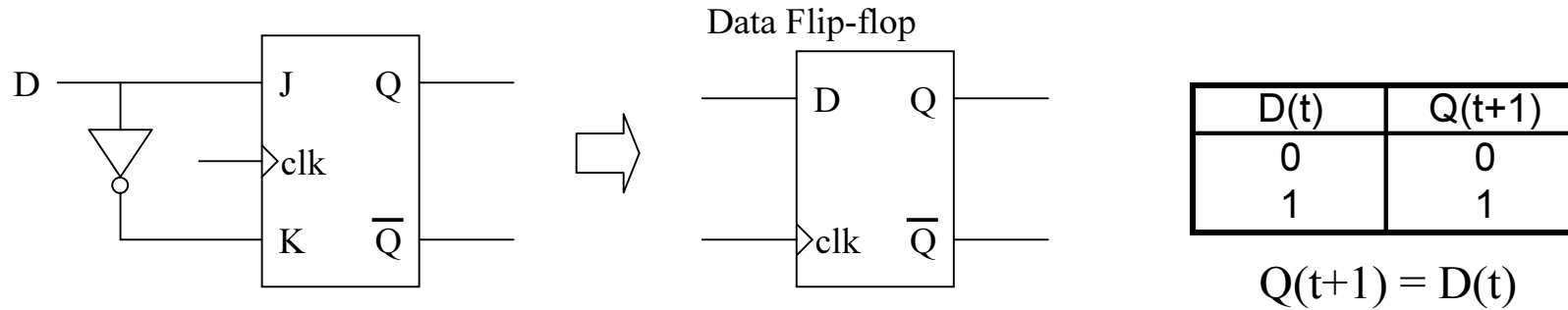


$Q(t+1) = D(t)$

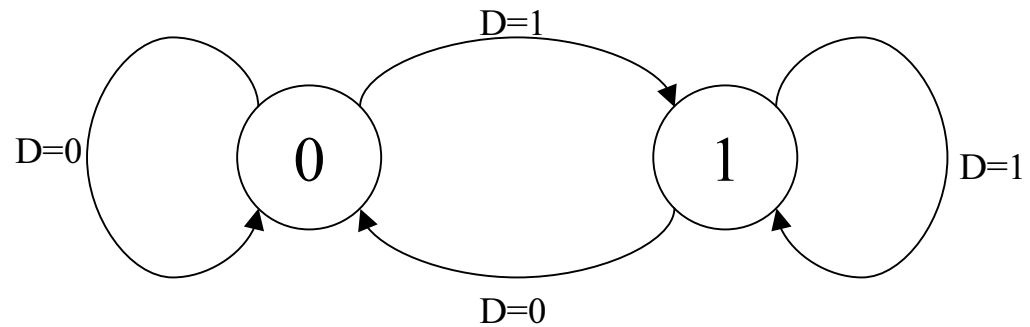

# State diagrams - examples

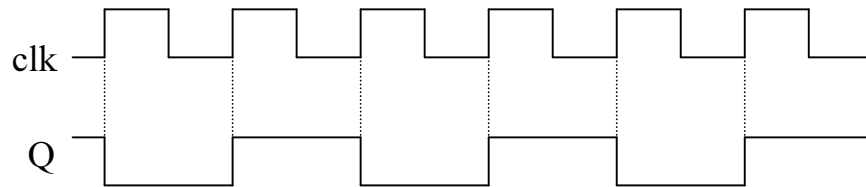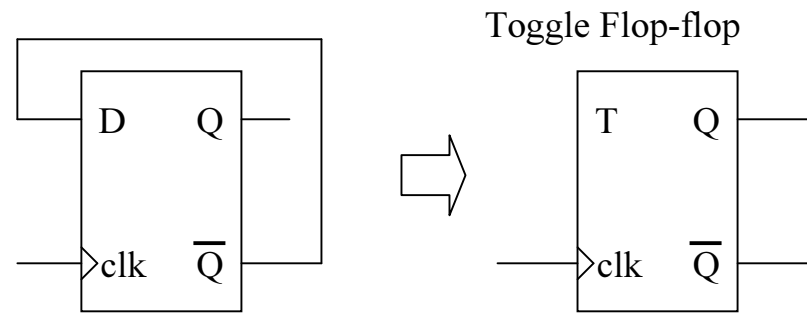


$$Q(t+1) = \bar{Q}(t)$$

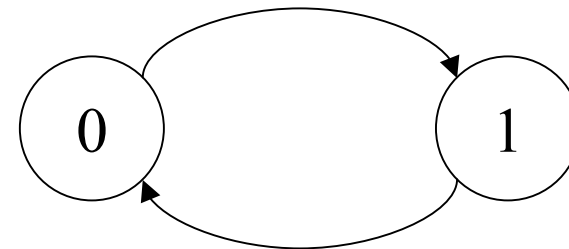



# State diagrams - examples

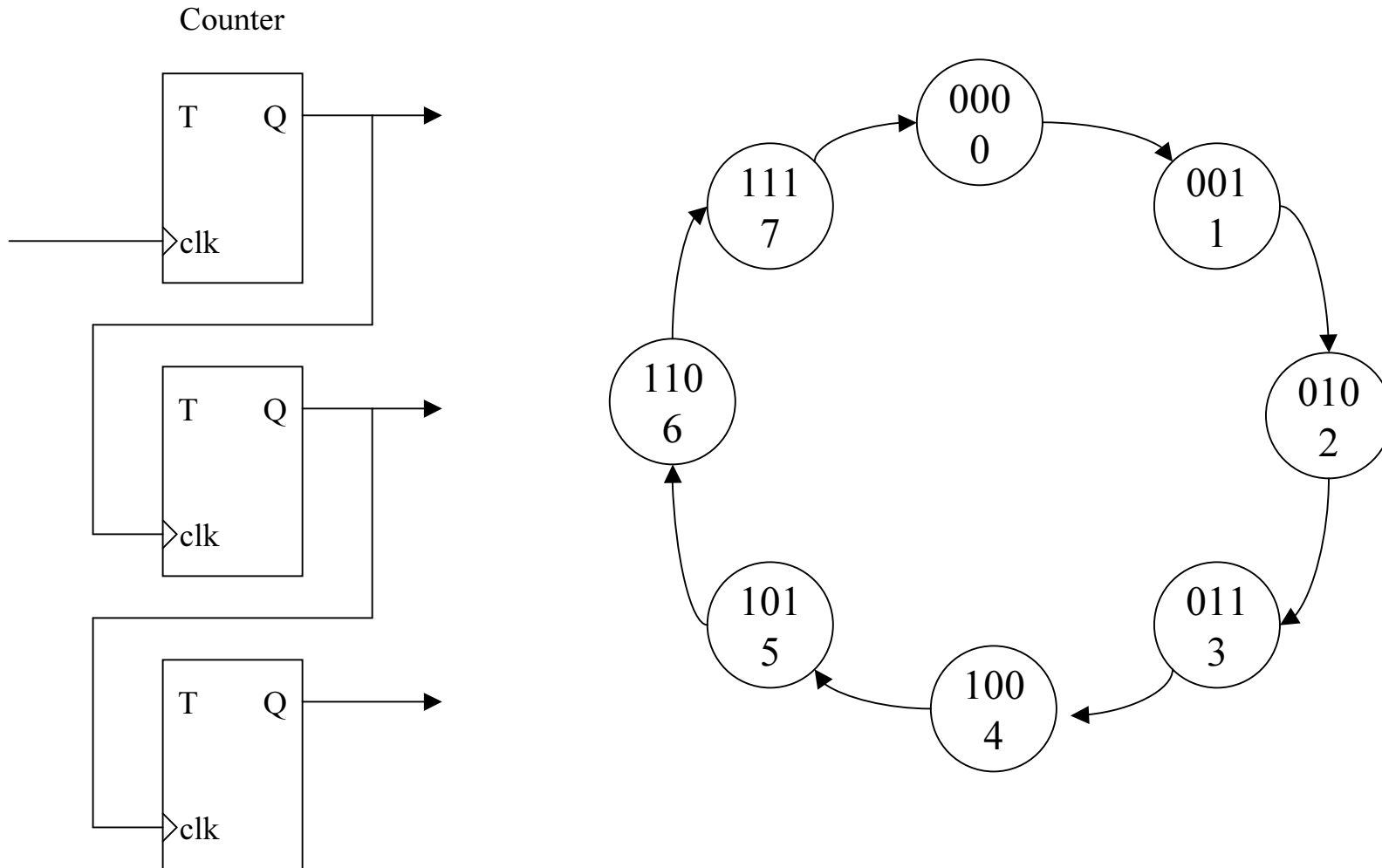

# State diagram - examples

